

# Assignment 11-Presentation

S.Manasa

IIIT Raichur

January 6, 2021

# Overview


## 1 Question

## 2 Solution

- Introduction
- Expressions
- Table
- Answer

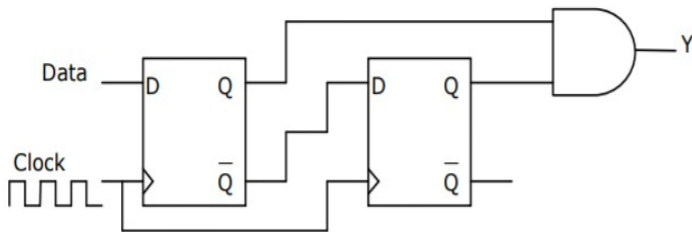
## Question GATE EC 2011-19

When the output Y in the circuit below is '1', it implies that the data has



- (A) changed from 0 to 1
- (B) changed from 1 to 0
- (C) changed in either direction
- (D) not changed

# Solution

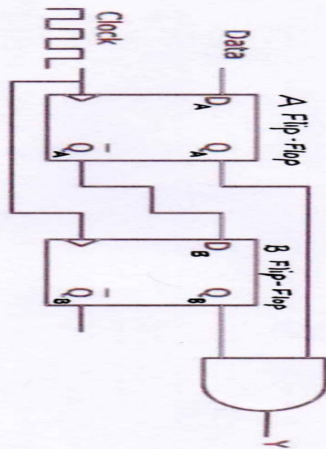

Figure

# Solution

In this problem there are two D-flip flops and one and gate. The output of and gate is Y which is the output of the above sequential circuit.

For our convenience let us take the first flip flop as A flip flop and second flip flop as B flip flop.

For A flip flop

- Input is  $D_A$
- Outputs are  $Q_A$  and  $\overline{Q_A}$

For B flip flop

- Input is  $D_B$
- Outputs are  $Q_B$  and  $\overline{Q_B}$

Now we need to find out the change in data when output Y is equal to 1.

# Solution

From the figure , it is clear that

$$Q_A = D_A = Data \quad (1)$$

$$Q_B = D_B = \overline{Q_A} \quad (2)$$

$$Y = Q_A \cdot Q_B \quad (3)$$

# Solution

Clock	Data	$Q_A$	$Q_B$
-		0	0
1st Pulse	$D_1$	$D_1$	1
2nd Pulse	$D_2$	$D_2$	$\overline{D_1}$

- When the clock is not given to the flip flops then  $Q_A$  and  $Q_B$  will remain in their reset state
- For the first clock pulse , we give the data as  $D_1$ 
  - From equation (1) we get  $Q_A = \text{Data}$ . Since data =  $D_1$ ,  $Q_A = D_1$
  - From equation (2) we get  $Q_B = \overline{Q_A}$ . Since  $Q_A = 0$ ,  $Q_B = 1$
- For the second clock pulse , we give the data as  $D_2$ 
  - From equation (1) we get  $Q_A = \text{Data}$ . Since data =  $D_2$ ,  $Q_A = D_2$
  - From equation (2) we get  $Q_B = \overline{Q_A}$ . Since  $Q_A = D_1$ ,  $Q_B = \overline{D_1}$

# Solution

Now we will generalise the case

- The output of first flip flop  $Q_A$  is equal to *present data*
- The output of second flip flop  $Q_B$  is equal to compliment of *previous data*

We know that  $Y = Q_A \cdot Q_B$

This means  $Y = (\text{presentdata}) \cdot (\overline{\text{previousdata}})$

So the output of Y is equal to 1 only when the present data is equal to 0. So the data must change from 0 to 1.

In this way option (A) is the correct answer



*Thank you for watching*

# The End